

Introduction to Verilog HDL


Chun-Wei Ku

sjerry@twins.ee.nctu.edu.tw

Dept. Electronics Engineering



National Chiao-Tung University

What is HDL?

 



- Hardware Description Language
 - Verilog-1995, Verilog-2001
 - VHDL
- Design complexity increases in the past 20 years
 - Gate counts increase
 - Complex algorithm in communication and multi-media
 - Design time and time-to-market pressure
- Why we use Verilog?
 - Easy for beginners
 - Adopted by more than 90% companies

HDL Design Flow

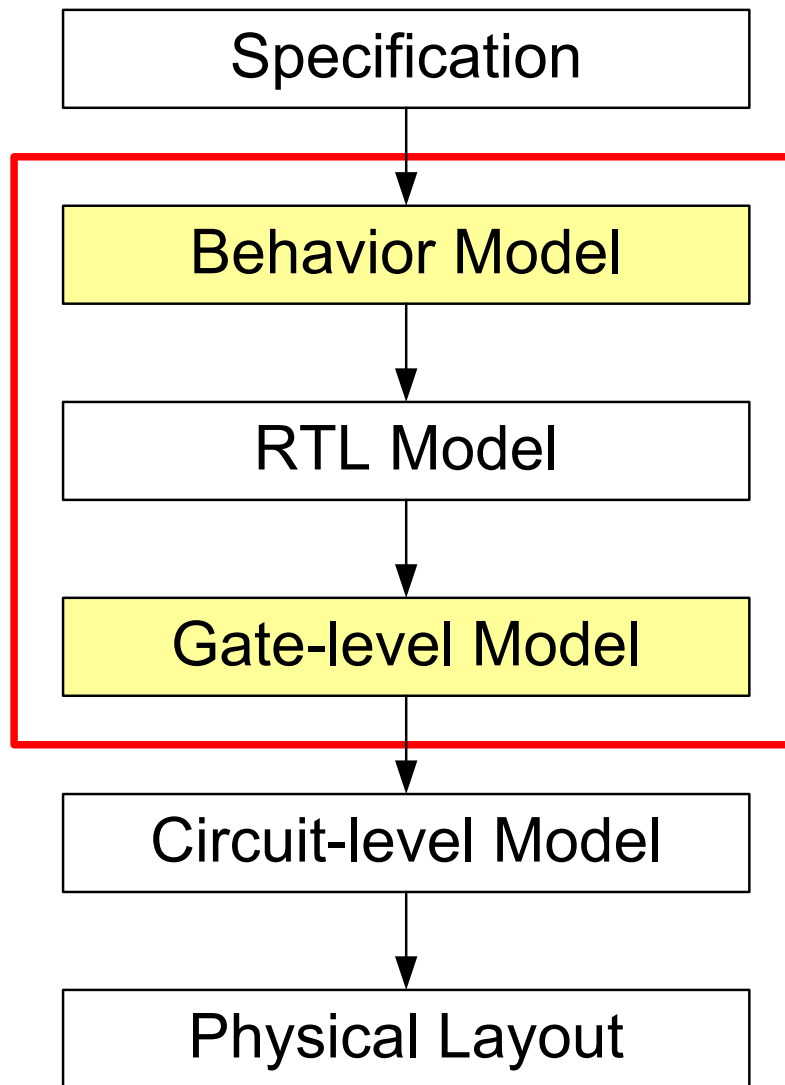 

**Verilog HDL
supported**


Module (1/2)

  

``include "file_name.v"`

- Similar to C/C++ function
 - top module => main()
- Using **``include`** to combine modules in different files
- A module has four parts
 - ***Port declaration***
 - ***Data type declaration***
 - ***Task & function declaration***
 - ***Module structure***

Module (2/2)

 

// Module Declaration

```
module FullAdder_1bit ( a, b, cin, sum, cout);
```

// Port Declaration

```
input  a, b, cin;  
output sum, cout;
```


// Data Type Declaration

```
wire    sum, cout, tmp;
```

// Module Structure

```
xor      #(5, 5) ( tmp, a, b );  
xor      #(5, 5) ( sum, tmp, b );  
.....  
  
endmodule
```

Data Type

 


- Declaration Syntax

`<data type> [msb:lsb] <data name1>, <data name2>;`

- Example

```
wire [7:0]    a;      // 8-bit wire a with msb=a[7] and lsb=a[0]
wire [0:7]    b;      // 8-bit wire b with msb=a[0] and lsb=a[7]
wire         c, d;    // 1-bit wire c and 1-bit wire d
reg  [15:0]   x;      // 16-bit data storage element
integer      i;       // 32-bit signed integer i
real         cycle;   // real number cycle
```

Port

 

- Declaration Syntax

`<input / output / inout> [msb:lsb] <data name1>;`

- Port connection & Module Hierarchy

```
module ADD_R ( A, B, CI, S, CO);  
endmodule
```


// connected by ordering

```
ADD_R #(16) FA0( x, y, 1'b0, z, overflow);
```

// connected by name

```
ADD_R #(16) FA1( .A(x), .B(y), .S(z), .CI(1'b0), .CO(overflow) );
```



Gate-level Design (1/2)

 


- Logic Gate Syntax

`<gate> #([Tplh], [Tphl]) (out1, ..., in1, in2, ...)`

 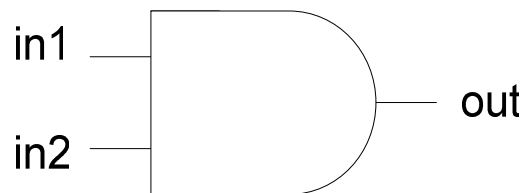- gate: and, or, xor, nand, nor, xnor, not, buf
- Tplh: rise time delay (0 to 1)
- Tphl: fall time delay (1 to 0)
- in/out: (out_port,in_port1,in_port2, ...)



Gate-level Design (2/2)

 

```
module Comb_logic(a, b, c, out);
```

```
input      a, b, c;
```

```
output    out;
```


```
wire      out, w1, w2;
```

```
and  #(0.2, 0.2) ( w1, a, b, c);
```

```
not  #(0.1, 0.1) ( w2, c);
```

```
or   #(0.2, 0.2) ( out, w1, w2)
```


```
endmodule
```

 

$$\text{out} = abc + c'$$

critical path delay = 0.4ns

Data Assignment (2/2)

 

- Number Format

`<bit_number>'<base><value>`

```
4'b0           // 4-bit 0000
4'b1001        // 4-bit 1001
8'b1111_1111   // 8-bit 1111 1111
16'hfe12       // 16-bit 1111 1110 0001 0010
9'o457         // 12-bit 100 101 111
8'd220         // 8-bit decimal 220
-8'd12         // 8-bit decimal -12
```