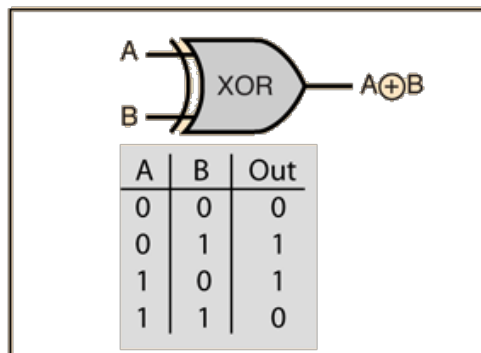


Exclusive OR Gate



The output is high when either of inputs A or B is high, but not if both A and B are high.

[How do you make one?](#)

[IC Example: IC 7486](#)

[Basic Gates](#)

[Index](#)

Reference:

[Tocci, Sec 4-6](#)

[Electronics concepts](#)

[Digital Circuits](#)

[HyperPhysics](#)*****[Electricity and magnetism](#)

R Nave

[Go Back](#)


Exclusive OR Gate

Logically, the [exclusive OR \(XOR\)](#) operation can be seen as either of the following operations:

$$1. A \oplus B = A\bar{B} + B\bar{A} \quad \text{A AND NOT B OR B AND NOT A}$$

$$2. A \oplus B = (A + B)(\overline{AB}) \quad \text{A OR B AND NOT A AND B}$$

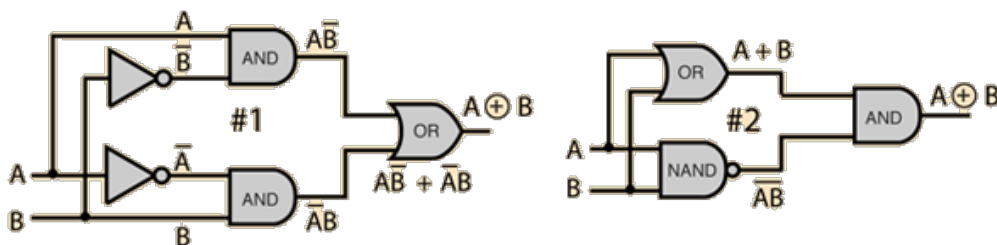which can be implemented by the gate arrangements shown. They can also be implemented using [NAND](#) gates only.



[Index](#)



Reference:

[Horowitz & Hill, Sec 8-12](#)

[Electronics concepts](#)

[Digital Circuits](#)

Basic Gates	
HyperPhysics ***** Electricity and magnetism	Go Back
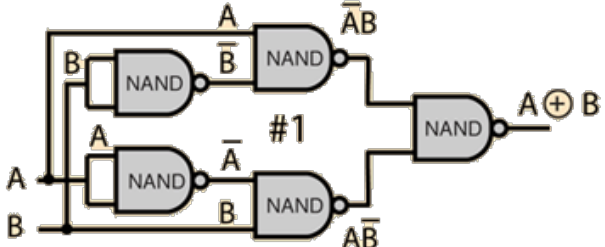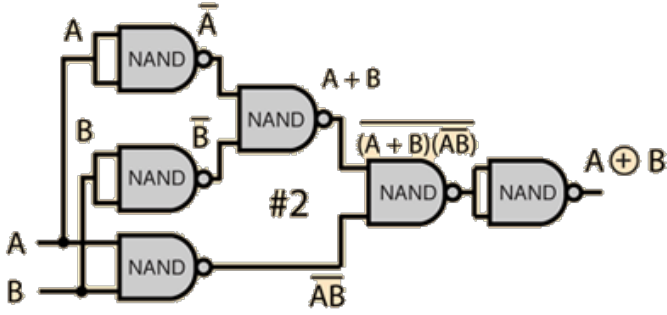
<h2 style="text-align: center;">Exclusive OR with NAND</h2> <div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;">  <p>#1</p> </div> <div> <p>The implementation of the exclusive OR (XOR) operation with just NAND gates illustrates the function of NANDs as universal gates.</p> </div> </div> <div style="display: flex; justify-content: space-around; align-items: flex-start; margin-top: 20px;"> <div style="text-align: center;">  <p>#2</p> </div> <div> <p>1. $A \oplus B = A\bar{B} + B\bar{A}$ A AND NOT B OR B AND NOT A</p> <p>2. $A \oplus B = (A + B)(\overline{AB})$ A OR B AND NOT A AND B</p> </div> </div> <div style="text-align: center; margin-top: 20px;"> DeMorgan's Theorem </div> <div style="text-align: center; margin-top: 10px;"> Basic Gates </div>	<p>Index</p> <p>Horowitz & Hill, Ch 8</p> <p>Electronics concepts</p> <p>Digital Circuits</p>
HyperPhysics ***** Electricity and magnetism	Go Back


IC 7486 Exclusive-OR

This is an example of convenient packaging of [XOR gates](#) in

[Index](#)

[Electronics concepts](#)

integrated circuit form.

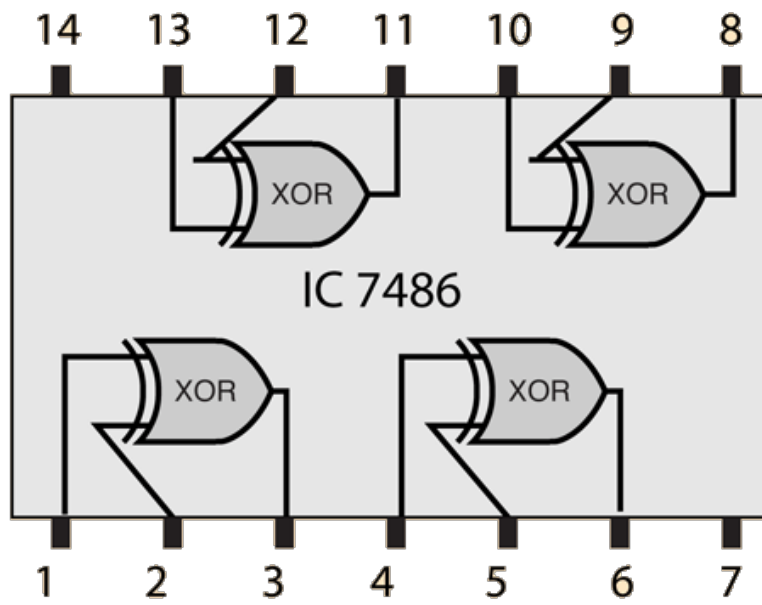

[Basic Gates](#) [IC Logic Circuits](#)

[Digital Circuits](#)

[HyperPhysics](#)*****[Electricity and magnetism](#)

R Nave

[Go Back](#)