

Subject index

- abbreviations, 10–11
- active filter, 150–3
- ADC, 4, 31, 46–50, 63, 69, 112, 125, 137–8
 - flash, 9, 47, 69
- algorithm, 4, 11, 160
- aliasing, 156
- amplifier
 - audio, 192
 - deflection, 90, 95, 101–9
 - direct-coupled, 90–2
 - feedback, 94
 - instrumentation, 127
 - intermediate frequency, 90
 - low noise, 190
 - operational, 5, 40, 47, 51–2, 69, 91, 94, 98, 104, 113–14, 116, 121, 123, 134, 136, 144–6, 150, 153, 157, 162, 190–3, 207–8
 - precision, 119, 143
 - repeater, 90, 195, 200–3
 - sense, 55
 - video, 91
 - wide-band, 6, 86, 90, 109, 114
- astable, 184–5
- attenuator
 - input, 77
 - networks, 73
 - pads, 73, 84
 - switched, 74
- balanced mixer, 179
- balun, 36–8, 87
- band-gap reference, 135, 143, 184
- base spreading resistance, 209
- bilateral switch, 140–1
- bipolar process, 133, 184
- Boltzmann constant, 188
- bootstrap, 129, 134
- capacitor
 - non-linearities, 127–8
- MOS, 136–7
- cascode, 7–9, 128
- CCD, 210
- charge
 - balancing circuitry, 143, 155
 - conservation, 136
 - control equations, 106
 - dispensing, 185
 - pumping, 138, 146, 149
- circuit shape, 1, 4, 7, 9, 12, 57, 86, 90, 94–5, 101–3, 121, 127, 175, 178, 181, 185, 210
- clock input, 55, 141
- CMOS, 9, 58, 136–8, 140–1, 163, 181, 184
- comparator
 - fast, 116, 131–4
 - gain-bandwidth, 133
- comparator circuits, 46, 132
- computer aided design, 202
- CRT, 2, 90, 95, 101, 123, 126
- current
 - comparator, 85
 - measurement, 72
 - mirror, 5, 181
 - source, 113
 - transformer, 83–5
- DAC, 111–12, 134, 137–8
- diffusion constant, 18
- diffusion length, 18
- diode
 - array, 38, 114–18, 120
 - bridge, 34
 - charge storage, 14
 - clamp, 21, 35
 - gallium arsenide, 44
 - sampling gate, 33
 - Schottky, 44
 - silicon, 15, 114, 126
 - snap-back, 14
 - snap-off, 14

- step recovery, 14–21, 123
- switch, 117, 177
- tuning, 21, 23–4
- varicap, 21
- Zener, 114, 116, 119, 126, 130, 141
- directional bridge, 87, 205
- directional coupler, 85, 195
- dynamic measurements, 64
- dynamic microphone, 192
- dynamic offset, 68
- dynamic range, 43
- electronic cooling, 207–9
- electronic instrumentation, 1–4, 194
- EMC, 187, 211
- feedback, 93, 109
 - general, 145
 - negative, 91, 94, 133, 195–7
 - positive, 52–5, 114, 129
 - resistors, 121, 193, 200
 - series, 94–6, 200
 - shunt, 94–6
 - stability, 145–6
- filter
 - bandpass, 150–7
 - biquad, 155
 - lead-lag, 169
 - low-pass, 149, 160, 165, 175
 - switched capacitor, 149–56
 - tracking, 159
- frequency divider, 149, 179
- frequency response, 29, 41, 81
- frequency synthesis, 112, 159, 179
- frequency to voltage converter, 139, 141
- function generator, 112
- gain-bandwidth product, 15, 94, 133
- gain enhancement, 9
- gallium arsenide, 7, 44, 58, 82, 157
- gate
 - exclusive OR, 163, 176
 - sampling, 25, 32
 - series/shunt, 35
- generator
 - fast ramp, 124
 - function, 112
 - noise, 206
 - precision ramp, 127
 - pulse, 111
 - sampling pulse, 12
 - signal, 112
 - timebase, 123–31
 - waveform, 111
- Gestalt, 4
- ground plane, 115–16, 132
- Hall sensor, 85
- human ear, 188, 194
- hybrid circuits, 21, 25, 31, 82
- hysteresis, 53–4, 59, 61–4, 69–70
- input bias current, 92, 117, 127
- input capacitance, 74, 77
- input circuit, 44, 75, 85, 92
- input power, 194
- integrator, 114, 134, 146, 161
- jitter, 15, 168, 174
- krytron, 15
- Laplace transform, 144, 161
- level
 - control, 119
 - d.c., 11
 - shifting, 58, 95–6, 98
- long tailed pair, 5, 7, 51, 96, 121
- mesa, 19
- microprocessor, 9, 111
- minority carrier lifetime, 106
- monostable, 13
- multiplier, 163, 176–7
- multivibrator, 13, 185
- mu-metal, 192
- noise
 - equivalent circuit, 189
 - figure, 189, 206, 209
 - flicker, 189, 191, 210
 - low frequency, 189, 210
 - generators, 206
 - magnetic, 192–3
 - measurements, 206
 - power, 189, 209
 - shot, 188
 - spectral density, 190
 - thermal, 187
- optical fibre, 72
- optimum source impedance, 189, 191, 210
- opto-electronic switch, 33
- oscillator
 - crystal, 112, 180
 - relaxation, 165
 - voltage controlled, 9, 118, 146, 149, 159, 181, 184–5
- oscilloscope, 2, 72
 - analog, 2, 79, 90–1, 101, 123
 - digitizing, 3, 30, 44, 46, 69, 79, 83, 90
 - sampling, 3, 29, 42
- OTA, 197–200
- PC, 3
- phase detector, 159
 - circuit shapes, 175–81
 - digital, 160, 180

- type I, 163, 175
- type II, 170, 175
- type III, 174–5
- PLA, 48–9
- plasma etching, 20
- PLL, 11, 140, 159
 - applications, 159
 - capture, 166
 - damping, 168
 - digital, 160, 181
 - integrated circuit, 162
 - theory, 159
- power gain, 79, 194
- power measurements, 72, 85
- probes, 72
 - active, 79, 81
 - current, 82, 85
 - errors, 78
 - high impedance, 66, 74–7, 99
 - passive, 74, 82
 - voltage, 74, 79
- process technique, 185, 189, 194
- propagation delay, 69, 124–5, 133
- pulse generator, 13
- pulse height analyser, 47
- pulse sampling, 12, 31, 43
- pulse transformer, 36
- pulse width, 13
- Q , 153, 155–6, 184
- radar receivers, 90
- radar signals, 33
- S -parameters, 85
- sample and hold, 27, 64, 211
- Schottky barrier, 7, 44
- Schmitt trigger, 53
- slew rate, 105, 119, 123–4, 134
- soft front panel, 3
- speed control, 159
- stereo decoding, 159
- surface states, 210
- switched capacitor
 - charge pump, 138
 - circuits, 136
 - filter, 149
 - voltage divider, 137
- symbols, 10–11
- symmetry, 54
- synchronization, 183
- television, 91
 - colour, 159
 - high definition, 210
 - receivers, 90
- thermometer code, 49
- thyatrons, 15
- time, 44
- attributed, 29
- base transit, 107
- carrier life, 106
- fall, 12, 24, 109, 111–12, 133
- rise, 12, 24, 30, 109, 111–12, 133
- sampling, 27
- storage, 16
- turn-off, 17
- track and hold, 30
- transformer
 - audio 192
 - balanced to unbalanced, 36–8
 - current, 83
 - feedback, 195–200
 - wide bandwidth, 87
- transient analysis, 106
- translinear circuits, 122
- transmission line, 14, 22, 31–2
 - balanced, 25, 36
 - coaxial, 25, 38
 - twisted pair, 37–8, 87–8
- transistors
 - array of, 10, 59, 96, 203
 - avalanche, 15
 - bipolar, 1, 51, 127, 188, 209
 - dual, 92, 98
 - FET, 7, 120
 - JFET, 1, 92, 94
 - lateral, 101
 - low noise, 209
 - MOS, 1, 33, 40, 92, 127–8, 140, 153
 - used in parallel, 209
- TRI-STATE, 171, 179
- varactor, 21, 184
- VCO, 9, 118, 146, 149, 159, 181, 184–5
 - as integrator, 161, 173
 - circuit shapes, 181–4
- VDU, 3
- virtual earth, 113, 116–18, 125, 134, 139, 143, 146, 150, 152
- VLSI, 9, 58, 137
- voltage
 - clamping, 183
 - measurement, 72
 - reference, 120, 127
 - to frequency converter, 119, 144–9
- waveform
 - conversion, 121, 131
 - fundamental, 112
 - generator, 111
 - sawtooth, 144, 175, 180
 - sine, 112
 - square, 112–13, 131
 - timebase, 123–31
 - triangle, 113, 121, 175, 180
- waveguide, 72