

# Contents

<i>Preface</i>	<i>xv</i>
<i>Acknowledgments</i>	<i>xix</i>
<b>1. Analog Filter: Concepts</b>	<b>1</b>
1.1 Introduction	1
1.2 Network Functions	2
1.2.1 Transfer function	4
1.3 Basic Filtering Action	5
1.3.1 Types of filters	6
1.4 From Passive to Active Filtering	9
1.5 Active RC Filters	11
1.5.1 Active R and active C filters	13
1.6 Sensitivity Concepts	13
1.7 Operational Amplifier	14
1.7.1 Analysis of circuits using operational amplifiers	16
1.8 Integrators Using Operational Amplifiers	17
1.9 Passive Components in Monolithic Filters	19
<i>References</i>	21
<i>Practice Problems</i>	21

<b>2. First- and Second-order Filters</b>	<b>25</b>
2.1 Introduction	25
2.2 First-order Filter Sections	25
2.3 Active First-order Filters	27
2.3.1 Use of inverting amplifiers	27
2.3.2 Bass cut/boost and treble cut/boost filters – application example	29
2.3.3 Fluorescence spectroscopy: application example	32
2.3.4 Use of non-inverting amplifiers	35
2.4 Effect of Operational Amplifier's Pole on Integrators	37
2.5 Biquadratic Section: Parameters $\omega_o$ and $Q_o$	42
2.6 Responses of Second-order Filter Sections	44
2.7 Second-order Low Pass Response	44
2.7.1 Earthworm seismic data acquisition: application example	48
2.8 Second-order High Pass Response	49
2.9 Second-order Band Pass Response	51
2.10 Band Reject (BR) Response	55
2.11 Second-order All Pass Response	57
2.12 Effect of Operational Amplifier's Pole on Biquads	58
<i>References</i>	59
<i>Practice Problems</i>	59
<b>3. Magnitude Approximations</b>	<b>63</b>
3.1 Introduction	63
3.2 Magnitude Approximations	64
3.3 Maximally Flat – Butterworth Approximation	66
3.3.1 Design of low pass Butterworth filter	69
3.3.2 Use of lossless ladder	70
3.4 Equal-ripple Approximations	74
3.5 Chebyshev Approximation	75
3.5.1 Low pass Chebyshev filter design	75
3.6 Inverse Chebyshev Approximations	79
3.6.1 Design of an inverse Chebyshev filter	81
3.7 Cauer or Elliptic Approximation	86
3.7.1 Design of Cauer filters	87
3.8 Maximally Flat Pass Band with Finite Zeros	95
<i>References</i>	97
<i>Practice Problems</i>	97

<b>4. Delay: Approximation and Optimization</b>	<b>101</b>
4.1 Introduction	101
4.2 Delay	102
4.3 Bessel Polynomial	104
4.4 Design of Bessel Filters	106
4.5 Delay Equalization	110
4.6 Delay Equalization Using First-order Sections	110
4.7 Delay Equalization Using Second-order Sections	114
<i>Practice Problems</i>	123
<b>5. Frequency and Impedance Transformations</b>	<b>125</b>
5.1 Introduction	125
5.2 Frequency and Impedance Scaling	126
5.2.1 Frequency scaling	126
5.2.2 Impedance scaling	127
5.3 Low Pass to High Pass Transformations	130
5.4 Low Pass to Band Pass Transformation	134
5.4.1 Design steps for transformation to BPF	139
5.4.2 Low pass to band pass network transformation	141
5.5 Low Pass to Band Reject Transformation	143
<i>Practice Problems</i>	145
<b>6. Sensitivity of Active Networks</b>	<b>149</b>
6.1 Introduction	149
6.2 Single-element (Incremental) Sensitivity	150
6.2.1 Semi-relative sensitivity	157
6.3 Transfer Function Sensitivity	158
6.4 Second-order Filter Sensitivities	160
6.5 Sensitivity Considerations for High-Order Active Filters	164
6.5.1 Simulation of LC ladder method	165
6.5.2 Sensitivity in cascade design	166
6.6 Multi-parameter Sensitivity	166
<i>Practice Problems</i>	167
<b>7. Single Amplifier Second-order Filters</b>	<b>170</b>
7.1 Introduction	170
7.2 Single-feedback Basic Biquadratic Section	171
7.2.1 Signal conditioning modules: application example	177

7.2.2	Bridged twin-T RC network	179
7.3	Multiple Feedback Single Amplifier Biquad (SAB)	182
7.3.1	Power line communication: automatic meter reading	185
7.4	Differential Input Single Amplifier Filter Sections	189
7.4.1	Differential input single feedback biquad	189
7.4.2	General differential input single OA biquad	191
7.5	General Active RC Feedback Single Amplifier Biquad	195
7.6	Coefficient Matching Synthesis Technique	198
7.7	Sallen and Key Biquad	199
7.7.1	Micro air vehicle: a case study	203
7.8	Delyiannis–Friend Biquad	204
7.8.1	Enhanced-Q circuit	206
	<i>References</i>	209
	<i>Practice Problems</i>	210
<b>8.</b>	<b>Multi Amplifier Second-order Filter Sections</b>	<b>213</b>
8.1	Introduction	213
8.2	State Variable Multi Amplifier Biquad	214
8.3	Tow–Thomas Biquad	215
8.4	Active Compensation for Inverting Integrators	218
8.4.1	Compensation for a non-inverting integrator	220
8.5	Ackerberg–Mossberg Biquad	221
8.6	Multi-output Biquad Using Summing Amplifier	223
8.6.1	Biquad using modified summation method	228
8.6.2	Active noise control: application example	231
8.7	Generalized Impedance Converter Based Biquad	233
8.7.1	General biquad using generalized impedance converter	236
	<i>References</i>	240
	<i>Practice Problems</i>	240
<b>9.</b>	<b>Direct Form Synthesis: Element Substitution and Operational Simulation</b>	<b>244</b>
9.1	Introduction	244
9.2	Gyrator and Inductance Simulation	246
9.3	Impedance Converters Using Operational Amplifiers	248
9.4	Antoniou’s Inductance Realization	249
9.5	Filter Realization Using Inductance Simulation	252
9.6	Floating Inductance Simulation	254
9.7	Generalized Inductance Simulation	257

9.8	Filter Realization Using FDNR	261
9.9	Principle of Operational Simulation	264
9.10	Operational Simulation of a Low Pass Ladder	269
9.11	Operational Simulation of the Band Pass Ladder	277
9.12	General Ladder Realization	284
9.12.1	Realization of shunt arm	286
9.12.2	Realization of series arm	289
	<i>References</i>	295
	<i>Practice Problems</i>	296
<b>10.</b>	<b>Cascade Approach: Optimization and Tuning</b>	<b>299</b>
10.1	Introduction	299
10.2	Cascade Design Basics	300
10.3	Optimization in Cascade Process	307
10.3.1	Pole-zero pairing	308
10.3.2	Section ordering	310
10.3.3	Gain assignment	313
10.4	Tuning of Filters	329
10.4.1	Automatic tuning	331
	<i>References</i>	331
	<i>Practice Problems</i>	332
<b>11.</b>	<b>Amplification and Filtering in Biomedical Applications</b>	<b>334</b>
11.1	Introduction	334
11.2	Instrumentation Amplifiers	335
11.3	Differential Biopotential Amplifier	336
11.3.1	Integrated circuit monolithic instrumentation amplifier	338
11.4	Physiological Signals	341
11.5	Analog Front-end for ECG Signal	343
11.5.1	An AFE system with low power on-chip filter	344
11.5.2	ECG signal acquisition system: an application example	346
11.6	Filtering of Surface Electromyography Signals	348
11.7	Brain-Computer Interface Application	350
11.8	Chamber Plethysmography	353
11.9	C-Message Weighting Function	355
	<i>References</i>	356
	<i>Practice Problems</i>	358

<b>12. Audio Signal Processing and Anti-aliasing Filters</b>	<b>360</b>
12.1 Introduction	360
12.2 Improvement in Audio Performance	361
12.2.1 Active crossover networks for loudspeakers	362
12.2.2 Infrasonic and ultrasonic filters	364
12.3 Satellite/Subwoofer Speaker Systems	367
12.4 Four Band Programmable Equalizer	370
12.5 Record Industry Association of America (RIAA) Equalization	373
12.5.1 RIAA phono pre-amplifier	374
12.5.2 Simultaneous cut and boost circuit	376
12.6 Phase Delay Enhancement in 3D Audio	379
12.7 Anti-aliasing Filters	380
12.7.1 Digitally tuned anti-aliasing filter	383
12.8 Active Filters for Video Signals: A Case study [12.14]	384
12.9 Reconstruction Filter	386
12.9.1 Video line driver for consumer video applications	389
<i>References</i>	395
<i>Practice Problems</i>	396
<b>13. Follow the Leader Feedback Filters</b>	<b>398</b>
13.1 Introduction	398
13.2 Structure of the Follow the Leader Feedback Filters	399
13.2.1 Use of lossless integrator blocks	400
13.2.2 Use of lossy integrator blocks	404
13.3 Feed-forward Path Based FLF Structure	406
13.4 Shifted Companion FLF Structure	411
13.5 General FLF Structure	414
13.5.1 Primary resonator block technique	418
<i>Practice Problems</i>	422
<b>14. Switched Capacitor Circuits</b>	<b>424</b>
14.1 Introduction	424
14.2 Switched Capacitor Resistor	425
14.3 Switched Capacitor Integrators	426
14.4 MOS Switches	431
14.4.1 Finite resistance	431
14.4.2 Permissible clock frequency	431
14.4.3 Non-overlapping clock generation	432

14.4.4 Parasitic capacitances	433
14.5 Parasitic Insensitive Integrators	434
14.6 Sampled Data Switched Capacitor Filters	437
14.6.1 Sampled data integrators	438
14.7 Bilinear Transformation: Warping Effect	439
14.8 First-order Filters	441
14.9 Simulation of SC Networks	443
<i>Practice Problems</i>	450
<b>15. Operational Transconductance Amplifier-C Filters</b>	<b>453</b>
15.1 Introduction	453
15.2 Basic Building Blocks Using OTAs	454
15.2.1 Resistor simulation	454
15.2.2 Integrators	455
15.2.3 Current and voltage addition	459
15.2.4 Voltage amplifiers	460
15.3 First-order Sections	461
15.4 Single-ended to Differential Output Conversion	464
15.4.1 Differential floating resistance and integrators	467
15.5 Second-order OTA-C Filters	470
15.5.1 Two-integrator loop biquads	470
15.5.2 OTA-C biquads derived from active RC circuits	476
15.6 OTA-C Filters Derived from LC ladders	477
15.6.1 Element substitution scheme	477
15.7 Single-ended and Differential Floating Inductance	480
15.7.1 Floating capacitor simulation	482
15.7.2 Anti-aliasing filter for an ECG detection device	485
15.8 Operational Simulation Process	486
<i>References</i>	489
<i>Practice Problems</i>	489
<b>16. Current Conveyors and CDTA (Current Differencing Transconductance Amplifiers) Based Filters</b>	<b>493</b>
16.1 Introduction	493
16.2 Second Generation Current Conveyors (CCII $\pm$ )	494
16.3 Some Basic Building Blocks	496
16.4 Current Conveyor Based First-order Filters	498
16.5 Current Conveyor Based Second-order Filters	500

16.5.1 Wein bridge based structure	501
16.6 High Input Impedance Biquads Using CCIIs	504
16.7 Application of Voltage Following Property of CCs	507
16.8 Biquads Using Single Current Conveyor	511
16.9 Biquads Using Two or More Current Conveyors	514
16.10 Inductance Simulation Using Current Conveyors	521
16.11 Application of CDTA	528
16.11.1 Inductance simulation using CDTAs	531
16.11.2 Biquadratic circuits using CDTAs	533
<i>References</i>	534
<i>Practice Problems</i>	535
<b>17. Active R and Active C Filters</b>	<b>538</b>
17.1 Introduction	538
17.2 Basic Techniques in Active R Synthesis	539
17.3 Direct Form of Active R Synthesis	539
17.4 Inductance Simulation	540
17.5 Active R Frequency Dependent Negative Resistance (FDNR)	547
17.6 Active R Capacitors	551
17.7 Application of Direct Form Active R Synthesis Technique	555
17.8 Cascade Form Active R Synthesis	557
17.9 Biquadratic Section Using Two OAs	558
17.10 General Biquad Using Three OAs	563
17.11 Basic Techniques for Active C Synthesis	563
17.12 Active OA-C Simulation of Immittance Functions	563
17.13 OA-C Filters: Direct Form Synthesis	570
17.14 OA-C Filters: Cascade Approach	575
17.15 Second-order OA-C Filters	577
17.16 Cascade Design	582
17.17 Effect of OA's Non-idealness on Active R and Active C Filters	584
<i>References</i>	585
<i>Practice Problems</i>	586
<i>Index</i>	593