

Answers to problems

Chapter 1

1. (a) Source; 6 W. (b) 110 C; 330 J.
2. Sources: *A* and *E*. Sinks: *B*, *C*, and *D*. 27 W.
3. $9\ \Omega$; $1/2\ \text{S}$.
4. $V_{AE}=1\ \text{V}$; $V_{BE}=1\ \text{V}$; $V_{CE}=-0.5\ \text{V}$; $I_{AB}=0$; $I_{CB}=-0.3\ \text{A}$.
5. 0.624 J; 2.63 kV.
6. $+1/84\ \mu\text{F}$.
7. 1 H; 2 A; $-1/2\ \text{V}$; 8 J.

Chapter 2

1. 5 V; 40.8 m Ω .
2. (a) 700 V; 250 Ω . (b) 2.8 A; 4 mS.
3. 0.347 V; 0.207 V.
4. 104 V.
5. $(21V_1 - V_2)/109\ \text{A}$; $(12V_1 + 15V_2)/109\ \text{A}$; $(13V_1 - 11V_2)/109\ \text{A}$
 $1/109\ \text{A}$; $21/109\ \text{A}$; $18/109\ \text{A}$
 $2/21\ \text{V}$; $109/21\ \Omega$.
6. 11 V; $5\frac{1}{2}\ \text{V}$.
7. Four; two; $-5.37\ \text{V}$.
8. $1/2\ \text{A}$.
9. $18\frac{1}{3}\ \text{A}$; $71\frac{2}{3}\ \text{V}$.
10. $5\pi/4\ \mu\text{A}$.
11. 10 k Ω ; 30 k Ω .
12. 2 Ω ; 4.5 Ω .
13. $5/6\ \Omega$.
14. 40 m Ω (approx); 4 A (approx).
15. Minimum at third load point; $1.32 \times 10^{-4}\ \text{m}^2$

Chapter 3

1. $(E^2 + \frac{1}{2}E_m^2)/R$; $(E^2 + \frac{1}{2}E_m^2)^{1/2}$.
2. (a) $1/\sqrt{3}$; $2/\sqrt{3}$ (b) $1/\sqrt{2}$; $\pi/2\sqrt{2}$.
3. (a) $10 + j10 = 14.1/\underline{45}$; $0.05 - j0.05 = 0.07/\underline{-45}$.
 (b) $10 - j10 = 14.1/\underline{-45}$; $0.05 + j0.05 = 0.07/\underline{45}$.
 (c) $25.9 + j18.55 = 31.9/\underline{35.7}$; $0.25 - j0.18 = 0.031/\underline{-35.7}$.
4. $460 \cos \omega t$.
5. $144/\underline{33.7}$; 17.14Ω ; 109 mH ; $139 \mu\text{F}$.
6. 288 V .
7. 45° ; 45° .
8. $\omega = [(1/C_1 + 1/C_2 + 1/C_3)/L]^{1/2}$.
12. $4.26 \text{ k}\Omega$; 213 pF ; $39.2 \text{ k}\Omega$; 2.62×10^{-3} .
13. $1/(\omega_0^2 C_1 C_2 R) + j(1/\omega_0 C_1 + 1/\omega_0 C_2)$
15. $R + j(\omega L - 1/\omega C - 1/\omega C_1)$; $-j(\omega M - 1/\omega C_1)$.
16. $C_0/(1 + 1/Q^2)$.
17. 35.6 kHz ; 0.15 V .
18. (a) $20 + j20$; $2.83 \cos(10t - 45)$. (c) $\omega_1 = \sqrt{50}$; $\omega_2 = \sqrt{150}$.
19. 15.9 kHz

Chapter 4

1. (a) 43.6 W ; 129.2 W ; 61.7 W . (b) 234 W ; $+207 \text{ VAr}$. (c) 0.75 .
2. $-j1.77 \Omega$ or $+j7.69 \Omega$.
3. $66.7/\underline{-53.1} \text{ A}$; $82.1/\underline{6.1} \text{ kV}$.
4. (a) $21.5/\underline{-63.4} \text{ A}$; $9.57/\underline{53.13} \text{ A}$; $19.2/\underline{-36.9} \text{ A}$.
 (b) $5 + j10 \Omega$; $15 - j20 \Omega$. (c) $10 + j7.5 \Omega$.
5. 3.31 A ; 110 W ; 210 VAr .
6. $1.2/\underline{0} \text{ A}$; $0.4/\underline{180} \text{ A}$; $0.28/\underline{135} \text{ A}$.
7. (a) $237/\underline{-3.16} \text{ V}$. (b) $250/\underline{-3.8} \text{ V}$.
8. 96.5% ; 6.36 A . Readings on primary: 500 A ; 545 V ; 26 kW .
9. (a) 8Ω . (b) $1/4 \text{ A}$; $1/2 \text{ W}$. (c) $2\frac{1}{2} \text{ W}$; $17\frac{1}{2} \text{ W}$.
10. $2.1 \times 10^{-8} \text{ W}$; $2.8 \times 10^{-8} \text{ W}$; $13 \times 10^{-8} \text{ F}$.
11. Ratio = $1:11$; 1.25 mV .
12. (a) $10 - j12 \Omega$. (b) 19.4 W .
13. $R = 50 \Omega$; $X = 0 \Omega$; $1/2 \text{ W}$; $79.1 \mu\text{H}$; 317 pF .
14. $0.33 \mu\text{F}$ (Z_1), 0.33 mH (Z_2) or 0.33 mH (Z_1), $0.33 \mu\text{F}$ (Z_2). Ratio: 0.33 .
15. 11.1Ω .

Chapter 5

1. (a) $18.6/\underline{3.4} \text{ A}$; $18.6/\underline{-116.6} \text{ A}$; $18.6/\underline{123.4} \text{ A}$.
 (b) $32.1/\underline{-26.6} \text{ A}$; $32.1/\underline{-146.6} \text{ A}$; $32.1/\underline{93.4} \text{ A}$.
 (c) 0.894 .

- (d) 20.6 kW.
 (e) $(20 + j10)/3 \Omega$.
 2. 6.97 A.
 3. $15.6 \pm j25.6 \Omega$.
 4. (a) 231 A. (b) 0.986. (c) 94.7 kW.
 5. 7.19 kW; 5.74 kW.
 6. (a) $V_{ab} = 440/0 \text{ V}$; $V_{bc} = 440/-120 \text{ V}$; $V_{ca} = 440/120 \text{ V}$.
 $I_a = 24.7/-63.6 \text{ A}$; $I_b = 11.1/-36.8 \text{ A}$; $I_c = 35/124.6 \text{ A}$.
 $I_1 = 3.04/-90 \text{ A}$; $I_2 = 13.2/-47.5 \text{ A}$; $I_3 = 22/120 \text{ A}$.
 (c) $V_L = 478/0$.
 7. Power = $W - V^2 R/(R^2 + X^2)$.
 8. (a) 0.513 MW/line. (b) 65.4 MW. (c) 139 kV.
 9. 25.5 μF .
 10. 6.2 kV (line); 97.7%.
 11. 551 A; 400 V.

Chapter 6

1. 1.0 s. (a) 0.69 s; 3 s.
 2. (a) 12 mA; zero. (b) $i_c = 12e^{-20000t}$.
 (c) Zero; 12 V. (d) $360 \times 10^{-8} \text{ J}$. (e) $720 \times 10^{-8} \text{ J}$.
 3. $i_1 = \frac{V}{R_2} e^{-t/T}$; $i_2 = \frac{V}{R_1 + R_2} (1 - e^{-t/T})$; $i = i_1 + i_2$.
 $T = CR_1 R_2 / (R_1 + R_2)$; 0.342 mA; 0.25 mA.
 4. (a) $i_c = 10e^{-100t} \text{ A}$; $v_c = 200(1 - e^{-100t}) \text{ V}$.
 (b) $i_c = -10e^{-66.7t} \text{ A}$; $v_c(0.1) = -100 \text{ V}$.
 (c) $i_c = 15e^{-100t} \text{ A}$; $v_c = 100(2 - 3e^{-100t}) \text{ V}$.
 5. 2.3 ms (closing); 0.6 ms (opening).
 6. (a) $i_L = 8.94 \cos(10^3 t - 63.4) - 2e^{-500t} \text{ mA}$ (b) 140° .
 7. $(15t + 0.3) \text{ V}$; 0.3 V.
 8. (a) 0.833 mA; 0.833 mA; 0.833 V.
 (b) 0.833 mA; 0.833 mA; 0.833 V; -60 mA/s ; -30 mA/s ;
 1500 V/S.
 (c) 0.083 mA; -0.67 mA ; 2.33 V.
 9. $R_1 = R_2$; $L = CR_1^2$.
 10. $R > 2\sqrt{(L/C) - r}$.
 11. $\left[LCD^2 + \left(CR_3 + \frac{L}{R} \right) D + \frac{R_3}{R} + 1 \right] v_2(t) =$
 $\left[LCD^2 + \left(CR_3 + \frac{L}{R_1} \right) D + \frac{R_3}{R_1} \right] v_1(t)$
 where $R = R_1 R_2 / (R_1 + R_2)$

$A_1 e^{-\alpha_1 t} + A_2 e^{-\alpha_2 t}$ where α_1 and α_2 are given by:

$$\alpha_1, \alpha_2 = \left(\frac{R_3}{2L} + \frac{1}{2RC} \right) \pm \left[\left(\frac{R_3}{2L} + \frac{1}{2CR} \right)^2 - \frac{1}{LC} \left(1 + \frac{R_3}{R} \right) \right]^{1/2}.$$

12. $\frac{E}{2} [e^{-Rt/(L+M)} - e^{-Rt/(L-M)}].$

13. (a) $v_c(t) = 0.67 + e^{-\alpha t}(0.33 \cos \omega t + 3.35 \sin \omega t)$
where $\alpha = 0.75$, $\omega = 0.97$.

(b) $v_c(t) = 0.51 \cos(2t - 130) + e^{-\alpha t}(1.33 \cos \omega t + 4.93 \sin \omega t)$

$$i(t) = \frac{v_c(t)}{2} + \frac{1}{0.5} \frac{d}{dt} v_c(t).$$

14. (a) 0.1 mH; 200. (b) 200 k Ω .

16. $v_c(t) = 10(8 - 7e^{-0.318t})$;
 $i(t) = 1 + 3.5e^{-0.318t}$.

17. (a) $a = v_2(0)$; $b = 2i_L(0)$; $c = \frac{1}{2}[3v_1(0) + v_2(0)]$.
(b) $v_2(0) = 1$; $i_L(0) = 1$; $v_1(0) = 1$.

(c) $v_2(t) = 1 - e^{-t} - \frac{2}{\sqrt{3}} e^{-t/2} \sin \frac{\sqrt{3}}{2} t$.

18. $V(s) = \frac{10}{s^2} (1 - e^{-0.1s}) \frac{1}{s} e^{-0.1s}$

$$i(t) = \left[10C - \frac{10}{\omega} \sqrt{\left(\frac{C}{L} \right)} e^{-\alpha t} \cos(\omega t - \phi_1) \right] u(t) \\ - \left[10C - \frac{10}{\omega} \sqrt{\left(\frac{C}{L} \right)} e^{-\alpha(t-0.1)} \cos\{\omega(t-0.1) - \phi_1\} \right. \\ \left. + \frac{1}{\omega L} e^{-\alpha(t-0.1)} \sin \omega(t-0.1) \right] u(t-0.1)$$

where $\omega^2 = (1/LC) - (R/2L)^2$; $\phi_1 = \tan^{-1}(\alpha/\omega)$; $\alpha = R/2L$.

20. $V_2(s) = 0.5/[(s+4)(4s^2+4s+2)]$;
 $v_2(t) = (1/100)e^{-4t} + (1/2\sqrt{50})e^{-0.5t} \cos(0.5t - 98.1)$.

21. $v_0(t) = 5[e^{-\alpha_1 t} - e^{-\alpha_2 t}]u(t)$
 $- 5[e^{-\alpha_1(t-a)} - e^{-\alpha_2(t-a)}]u(t-a)$

where $\alpha_1 \approx 5 \times 10^{-3}$, $\alpha_2 \approx 2 \times 10^6$, $a = 5 \times 10^{-6}$.


23. $H(s) = 1/(s^3 + 2s^2 + 2s + 1)$.

24. $R(\min) = 2 \left[\frac{L}{C} (1+k) \right]^{1/2}$.


25. $F(s) = \frac{\alpha(s+\alpha) - \beta^2}{(s+\alpha)^2 - \beta^2}$.

Chapter 7

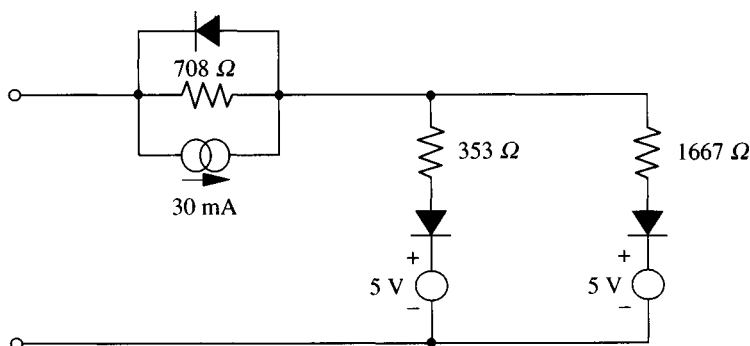1. 10.3 mA; 2.2 V.
2. 10.8 mA; 2.05 V; 19 mW; 0.8 mW.
3. 5.1 mA; 7.3 V; 2.4 V; 4.9 V; $R_{d.c.} = 1430 \Omega$; $R_{a.c.} = 788 \Omega$.
4. (a) $0.61 \text{ k}\Omega < R < 2.9 \text{ k}\Omega$. (b) -0.17 V or 0.46 V .
5. (a) 7 V. (b) 270Ω .
6. Slopes: 1, $\frac{1}{2}$, 0. Break points 1 V, 2 V.
7. Breakpoints: (8 V, 0 A) and (16 V, 2 A).
Slopes (i/v): $1/10$, $1/4$ and $7/20$ corresponding to resistance of 10Ω , 4Ω , 2.85Ω .
- 8.



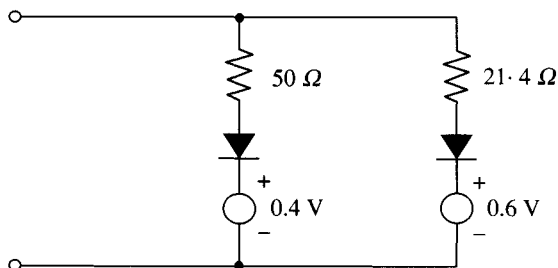9. $25.9/R$.
10. (a) 0.53 V; 2.3 mA; 1.2 mW. (b) 1.2 mW.



11. $R_1 = 1/3 \text{ k}\Omega$; $R_2 = 2/3 \text{ k}\Omega$; $R_3 = 3 \text{ k}\Omega$; $R_4 = 7/6 \text{ k}\Omega$; $R_5 = 1.46 \text{ k}\Omega$.
12. 0.712 A.
13. (a) 1.67 A; 1.87 V; 1.13 V. (b) 1.16 A; 1.58 V, 0.85 V; 0.58 V.
15. (a) $R_1 = \text{M}\Omega$; $R_2 = 28.6 \Omega$. (b) 0.1 mA; 31 mA.
16. (c) 10 mA. (d) 1.2 ms.

17. $v_c(t) = V(1 - \cos \omega_0 t)$, $0 < t < \pi/2\omega_0$
 $v_c(t) = V + \omega_0 r C V [e^{-\frac{r}{L}(t - \frac{\pi}{2\omega_0})} - e^{-\frac{1}{rC}(t - \frac{\pi}{2\omega_0})}]$,
 $t > \pi/2\omega_0$.
18. (a) 1.05 A. (b) $C = 0.1$ F.
19. (a) 56.3 mA. (b) 6.3%. (c) 0.73 A. (d) 0.187 A. (e) 3.2%. (f) 0.1%.
20. (a) 360 V; 9.6 V. (b) 262 V; 377 μ F.
21. (a) 25 mV. (b) $V_d = \sqrt{2[(V_r^2 + V_s^2 + 2V_r V_s \cos \phi)^{\frac{1}{2}} - (V_r^2 + V_s^2 + 2V_r V_s \cos \phi)^{\frac{1}{2}}]}$
22. 90° ; 16.9 k Ω
 $i = 3.24 \sin(\omega t - 17.4) - 18e^{-1000t}$ A ($t \geq 2.5$ ms). 107° ; 197°
23. $f(t) = \frac{4A}{\pi} \sum_{n=2k+1}^{\infty} \frac{1}{n} \left[\frac{\sin(n2\pi p/T)}{n2\pi p/T} \right] \sin \frac{n2\pi t}{T}$ $k=0, 1, 2, \dots$
 (c) $p = T/6$. (d) $p = T/10, T/5$.
24. 60° ; 1.15.

Chapter 8

1. $h_{11} = 14/3 \Omega$; $h_{12} = 1/3$; $h_{21} = -1/3$; $h_{22} = 1/12$ S.
3. $z_{11} = R_e + R_b$; $z_{12} = R_e$; $z_{21} = R_e - \beta R_d$; $z_{22} = R_d + R_e$.
4. $y_{11} = y_{22} = \frac{s(s+3)}{2s+1}$; $y_{12} = y_{21} = \frac{s(s+1)}{2s+1}$.
5. (a) $A = -\frac{1}{\mu}[1 + Y(Z + R_2)]$; $B = A/R_1$
 $C = -\frac{1}{\mu}[2Z + Z^2 Y + R_2(1 + ZY)]$; $D = C/R_1$
6. $y_{11} = y_{22} = \frac{R^2 C^2 s^2 + 4RCs + 1}{2R(RCs + 1)}$; $y_{21} = y_{12} = \frac{-R^2 s^2 C^2 + 1}{2R(RCs + 1)}$
 Infinite attenuation when $\omega = 1/RC$.
7. (b) $y_{12} = y_{21} = \frac{R^2 s^3 C^3}{2(1 + sRC)} = \frac{s^3 C T^2}{2(1 + sT)}$.
8. Iterative impedances: 21.3 Ω and 16.2 Ω .
 Image impedances: 17.1 Ω and 20.5 Ω .
9. $\frac{V_{IN}}{V_{OUT}} = \frac{1}{sL} [R + sL + \sqrt{(R^2 + 2RsL)}]$; $z_1 = \sqrt{(R^2 + 2RsL)}$
 For given values: $V_{IN}/V_{OUT} = 1.79 - j2.28$; $z_1 = 1270 + j790 \Omega$.