

Index

- 1N4148 diode, 409–414
- 1N5817 Schottky diode, 357–362
- 2N3553 npn transistor, 371–372
- 2N3906 pnp transistor, 373–378
- 2N4124 npn transistor, 379–384
- acoustics, 131
 - L_p (Sound Pressure Level), 134
 - transmission line analogy, 131–134
- active circuit, 142
- active region
 - BJT, 145–146
 - JFET, 249
- admittance, 57
 - normalized, 91
- alternating current (AC), 34
- Ampere's Law, 279
- amplifier, 10
 - audio, 245, 250–253
 - buffer, 18, 178–179
 - Class-A, 156–158, 180
 - Class-B, 180, 193–196
 - Class-C, 180, 182–185
 - Class-D, 188–189
 - Class-E, 190–192
 - Class-F, 192–193
 - common-emitter, 154–155, 182
 - differential, 168–170
 - driver, 18, 175–177
 - emitter follower, 166–168
 - power, 18, 185–188, 199–200
 - source follower, 174–175
- amplitude modulation (AM), 8
- antenna, 305–306
 - dipole, 283, 290–292
 - isotropic, 282
 - monopole (whip), 292–293, 305–306
 - receiving, 283–284
 - transmitting, 282–283
 - whip (monopole), 292–293, 305–306
 - Yagi, 293–294
- antenna gain, 282
- antenna loading, 293
- antenna noise, 266
- antenna theorem, 287–288
- Armstrong, Howard, inventor, 15
- attenuator, 39
- attenuator noise, 267
- audio amplifier, 245, 250–253
- automatic gain control (AGC), 17, 254–256
- autotransformer, 305
- available power, 39, 85
- bands, frequency, 7
- bandwidth, 13
- base, 143
- base resistance, 161–162
- beacons, radio, 306–308
- beat frequency oscillator (BFO), 16, 239–240
- bipolar junction transistor (BJT), 143–146
 - collection efficiency α , 144
 - current gain β , 144
 - regions of operation, 146
- Bode plot, 252
- bridge (full-wave) rectifier, 35
- brightness B , 288
- broad-band receiver, 231
- buffer amplifier, 18, 178–179
- Burdick, Wayne, designer, xiv, 1, 128
- Butterworth (maximally flat) filter, 97
- bypass capacitor, 178
- call signs, 310–311
- capacitor, 28, 152
- characteristic impedance, 75
- charge-storage delay, 185
- Chebyshev (equal ripple) filter, 97
- Chebyshev polynomial, 98
- Clapp oscillator, 207–210
- Class-A amplifier, 156–158, 180
- Class-B amplifier, 180, 193–196
- Class-C amplifier, 180, 182–185
- Class-D amplifier, 188–189
- Class-E amplifier, 190–191
- Class-F amplifier, 192–193

- Cohn (crystal) filter, 110–111
- collector resistance, 165
- common-collector amplifier (emitter follower), 166–168
- common-emitter amplifier, 154–155, 182
- comparator, 223
- complex numbers, 49
- conductance, 20, 57
- critical angle θ_c , 302
- critical frequency f_c , 299
- crystal, 107–108
- crystal oscillator, 214–217
- current, 4
- current divider, 26
- current mirror, 245–247
- cut-off frequency, 13
- cut-off voltage in a JFET V_c , 171

- D layer in ionosphere, 294–295
- decibels (dB), 10–11
- describing function, 213
- differential amplifier, 168–170
- diode, 33
 - pn, 34
 - Schottky, 34
 - snubber, 34, 47–48
 - varactor, 34, 210, 219
 - Zener, 34
- dipole antenna, 283, 290–292
- direct-conversion receiver, 13, 226
- direct current (DC), 34
- dispersion, 80
- distributed capacitance, inductance, 72
- driver amplifier, 18, 175–177
- driver transformer, 124–126
- drain, 171
- duty cycle, 193
- dynamic range (DR), 273

- E layer in ionosphere, 294–295
- Early voltage, 165
- effective area A , 284
- effective earth radius (8,500 km), 286–287
- effective length h , 283–284
- emitter degeneration, 162–166, 177–178
- emitter follower, 166–168
- equipment for measurements, 315
- Euler's formula, 53
- EZNEC antenna calculations, 294, 305

- F layers in ionosphere, 294–295
- fading, 261
- field-effect transistor (FET), 170–174, 191
- filter, 12
 - band-pass, 12, 104
 - band-stop, 104
 - Butterworth, 97
 - Chebyshev, 97
 - Cohn (crystal), 110–111
 - equal-ripple, 99
 - harmonic, 112–114
 - high-pass, 58
 - intermediate frequency (IF), 110–111, 114–118
 - ladder, 97–99
 - low-pass, 12, 57–59
 - notch, 89
 - radio frequency (RF), 16, 66–68, 126–130
 - transmit, 17, 68–70
- filter design, 100
- filter tables, 101
- Fourier coefficients, 329–331
 - narrow pulses, 333–334
 - rectified cosine, 332–333
 - square wave, 331–332
- frequency, 5
 - critical f_c , 299
 - cut-off, 13
 - fundamental, 184
 - image, 14, 230
 - intermediate (IF), 226
 - radio (RF), 13
 - resonant, 59, 62
- frequency modulation (FM), 8
- frequency-shift keying (FSK), 9
- Friis formula, 284–285
- full-wave (bridge) rectifier, 35
- fundamental frequency, 184

- gain,
 - amplifier, 10–11, 158–159
 - antenna, 282
- gain limiting, 211–214, 221–225
- gate, 171
- Gerke, Frederick, 308–309
- Gilbert Cell, 226–228
- ground, 2

- Hajimiri, Ali, 218
- half-wave rectifier, 34
- harmonic filter, 112–114
- harmonics, 184
- heterodyning, 11

- image frequency, 14, 230
- immitance, 101
- impedance, 56
 - characteristic, 75
 - inverter, 109–110

normalized, 91
parallel-to-series conversion, 65–66
wave, 280
inductance formulas, 119–120
inductor, 35
integrated circuit (IC), 142, 222
integrator, 58
interference, 261
intermediate frequency (IF), 226
intermodulation, 270–272
ionograms, 299–300
ionosphere, 294–297

Johnson noise, 261, 264–266
junction field-effect transistor (JFET),
170–174
as a variable resistor, 249

key clicks, 233–236
keying waveform, 243
Kirchhoff's laws, 2–5

L_p (Sound Pressure Level), 134
ladder filter, 97–99
large-signal transconductance G_m , 213
Lee, Tom, 218
lightning noise, 266
line-of-sight range, 285–287
linear region, JFET, 249
LM386N-1 audio amplifier, 245,
399–407
LM393N comparator, 223
look-back resistance, 26
loss, 13
loss resistance R_l , 280
loudspeakers, 138–140
lower-sideband receiver, 17
lumped element, 72

magnetizing current, 121, 123–124
masking of sounds, 136–137
maximum usable frequency (MUF), 301
Maxwell's equations, 278
Miller capacitance, 164
Minimum Detectable Signal (MDS), 262
Minimum Detectable Intermodulation
(MDI), 274
mixer, 11, 226
Product Detector, 16, 239–241
RF, 16, 237–239
transmit, 17, 242–244
mixer mathematics, 228–229
modulation, 8
monopole antenna, 292, 305–306

Morse, Samuel, inventor, 308
Morse code, 308–309
Morse code vocabulary, 312–313
MOSFET, 191
muting circuit, 257–258

Nahin, Paul, author, xiii, 19, 65, 92
noise, 261
antenna, 266
attenuator, 267
cascading components, 268
noise bandwidth, 276
Noise-Equivalent Power (NEP), 262
noise figure, 269
noise phasors, 263–264
noise power density (N), 262
noise temperature, 265–266
NorCal 40A transceiver kit, 315
normalized admittance, 91
normalized impedance, 91
Norton equivalent circuit, 23
Nyquist's noise formula, 264–267

Ohm's law, 20
open circuit, 23
operational amplifier (op amp), 247–249
golden rules, 248
oscillation criteria, 204
oscillator, 14
beat-frequency (BFO), 16, 239–240
Clapp, 207–210
Colpitts family, 207
crystal, 214–217
Hartley family, 207
synthesized, 210
transmit, 17, 242
variable-frequency (VFO), 16, 210,
219–221
oscillator starting conditions, 210

parallel resonance, 62, 68–70
parallel-to-series conversion, 65–66
pass band, 12
passive circuit, 142
peak voltage, 5–6
phase, 50
phase noise, 217
phase-shift keying (PSK), 9
phasing dots, 121
phasor, 53
noise, 263–264
wave, 77–78
phon, 134–135
plane wave, 279
polarization, 279

- power, 2, 5
 - available, 39, 85
 - average, 21
 - complex (phasor), 63
 - in transmission lines, 76–77, 85–86
 - reactive, 64
- power amplifier, 18, 185–188, 199–200
- prefixes, 3
- product detector, 239–241
- propagation, 306–308
- Puff* circuit simulator, 335–354
 - artwork, 353
 - component sweep, 353
 - device file format, 348
 - in *Windows*, 336–337
 - parts, 345
 - time-domain plots, 353
 - units in, 346
- push-pull amplifier, 188, 196
- Q (quality factor), 60–61, 63–65, 89–90
- RC circuits, 31, 57
- RL circuits, 37
- radiation resistance R_r , 280
- radio frequency (RF), 13
- radio frequency filter, 16, 66–68
- radio frequency mixer, 237–239
- radio waves, 278–280, 297
- reactance, 56
- receiver
 - broad-band, 231
 - direct-conversion, 13, 226
 - lower-sideband, 17
 - superheterodyne, 15, 226
 - triple-conversion, 232
 - upper-sideband, 17
- receiver-incremental tuning (RIT), 222
- receiver switch, 147, 149–151
- receiving antenna, 283–284
- reciprocity in antennas, 288–290
- rectifier, 34
 - half-wave, 34
 - full-wave (bridge), 35
- reflection coefficient ρ , 83
- refractive index n , 298
- rejection, 13
- resistance, 20, 56
- resonance,
 - parallel, 62, 68–70
 - series, 59, 66–68
 - transmission line, 86–89, 95–96
 - resonant frequency, 59, 62
- reverse active region, BJT, 146
- rms voltages, 137–138
- SA602AN mixer, 214, 237, 415–425
- saturation conductance, resistance, 147
- saturation current, 160
- saturation region
 - BJT, 146
 - JFET, 249
- scattering parameters, 340–341
- series resonance, 59, 66–68
- short-circuit, 24
- sidetone, 258
- signal-to-noise ratio (SNR), 261–262
- Snell's law, 301
- snubber diode, 34, 47–48
- solar flux, 296
- soldering, 66–67
- solid angles, 281
- Sound Pressure Level L_p , 134
- sounders for telegraphy, 308
- source follower, 174–175
- source resistance, 22
- source (transistor), 171
- sources,
 - dependent, 145
 - ideal, 23
- speakers, 138–140
- speed of light, 6
- spurious response ("spur"), 230
- steradians, 281
- superheterodyne receiver, 15, 226
- susceptance, 57
- standing wave ratio (SWR), 94, 141
- stop band, 12
- sunspot cycle, 296–297
- telegraphist's equations, 73–74
- temperature coefficients, 210–211
- thermal modeling (transistor), 196–198, 200–203
- thermal voltage V_t , 160
- Thevenin equivalent circuit, 23
- Thevenin's theorem, 26
- Titanic*, RMS, 1
- transatlantic telegraph cable, 82
- transconductance g_m , 162, 172, 213
- transformer, 120–121
 - driver, 124–126
 - ideal, 122–123
 - impedance, 122–123
 - tuned, 124, 126–130

- transistor,
 - bipolar-junction (BJT), 143–146
 - field-effect, (FET), 170–174, 191
- transistor switch, 146–149
- transmission coefficient τ , 83
- transmission line,
 - attenuation constant α , 79
 - dispersion, 80
 - equations, 73–74
 - high-resistance approximation, 82
 - large-reactance approximation, 81
 - load, 90
 - phase constant β , 77
 - power, 76–77, 85–86
 - propagation constant k , 79
 - quality factor Q , 89–90
 - resonance, 86–89, 95–96
 - zero-dispersion condition, 81
- transmit filter, 17, 68–70
- transmit mixer, 16, 242–244
- transmit oscillator, 17, 242
- transmit switch, 151–153
- transmitting antenna, 282–283
- triple conversion receiver, 232
- Uda, Shintaro, 293, 305
- units, 3
- upper-sideband receiver, 17
- Vail, Alfred, inventor, 308
- variable-frequency oscillator (VFO),
 - 16, 210, 219–221
- vendors for parts, 316
- virtual ground, 248
- voltage, 2
 - peak, 5–6
 - root-mean-square (rms), 137–138
- voltage divider, 25–26
- wave impedance, 280
- wave phasors, 77–78
- whip antenna, 292–293, 305–306
- Y factor for measuring noise, 270
- Yagi, Hidetsugu, 293
- Yagi antenna, 293–294